

Tutorial Works Series N° 5

Exercise 01:

- A. Let the transition table (excitation) of the JK flip-flop be below. Deduce the logic values of the variables J and K for each of the following outputs:



Q	Q ⁺	J	K
0	0		
0	1		
1	0		
1	1		

- B. From the truth table relating to the following JK flip-flop, give the different output values as well as the operating mode of the flip-flop:

Inputs			Outputs		Functioning
J	K	Q _n	Q _{n+1}	$\overline{Q}_{n+1}$	
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			


Exercise 02:

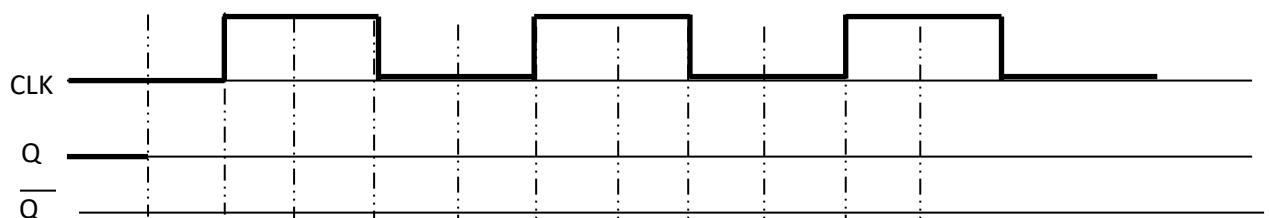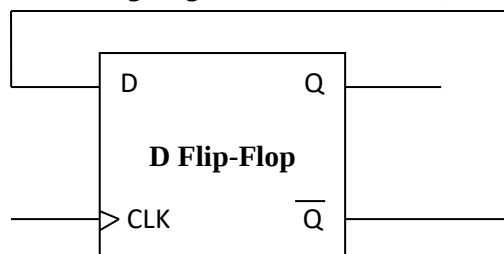1. Draw the timing diagram obtained from Q in the following figure:



2. Calculate the frequency (F_Q) of Q based on the frequency F_C of the CLK?

3. Draw the timing diagrams of CLK, Q0, and Q1 for the following figure:

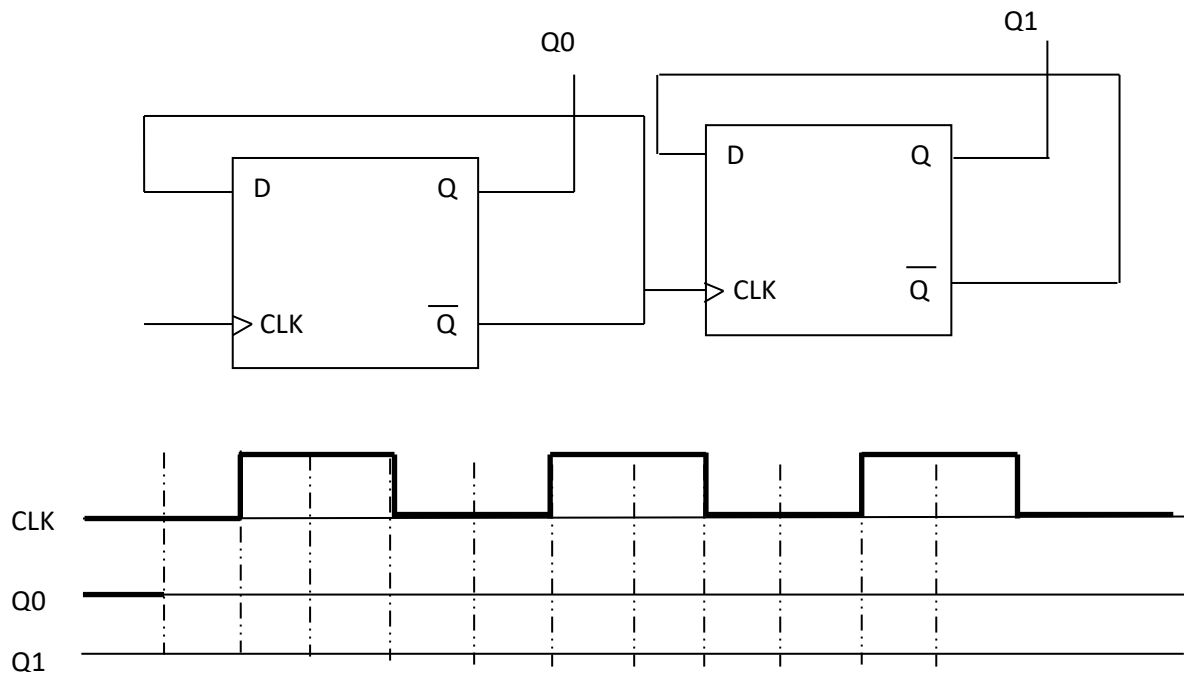

Exercise 03:

Complete the timing diagrams below for the following flip-flops:

